
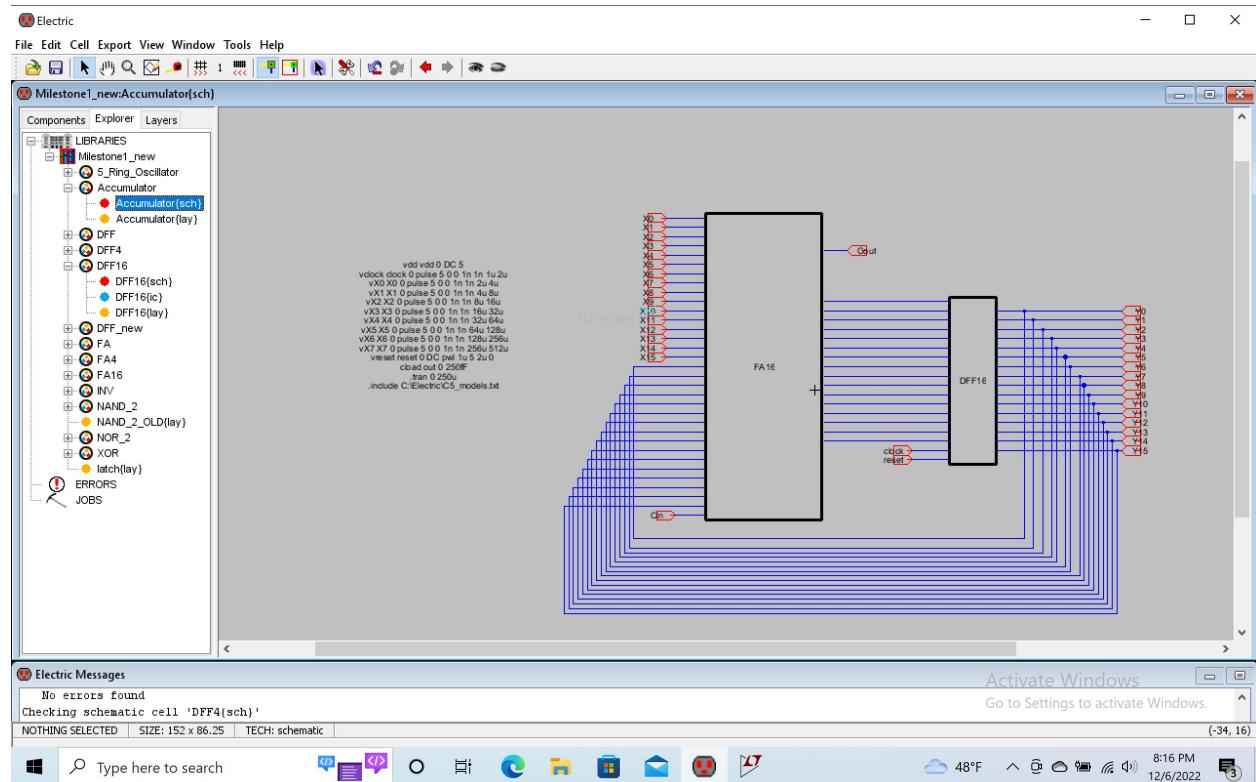


Cristobal Drogueyt
 EECE 574
 Final Project Integration


Accumulator Schematic

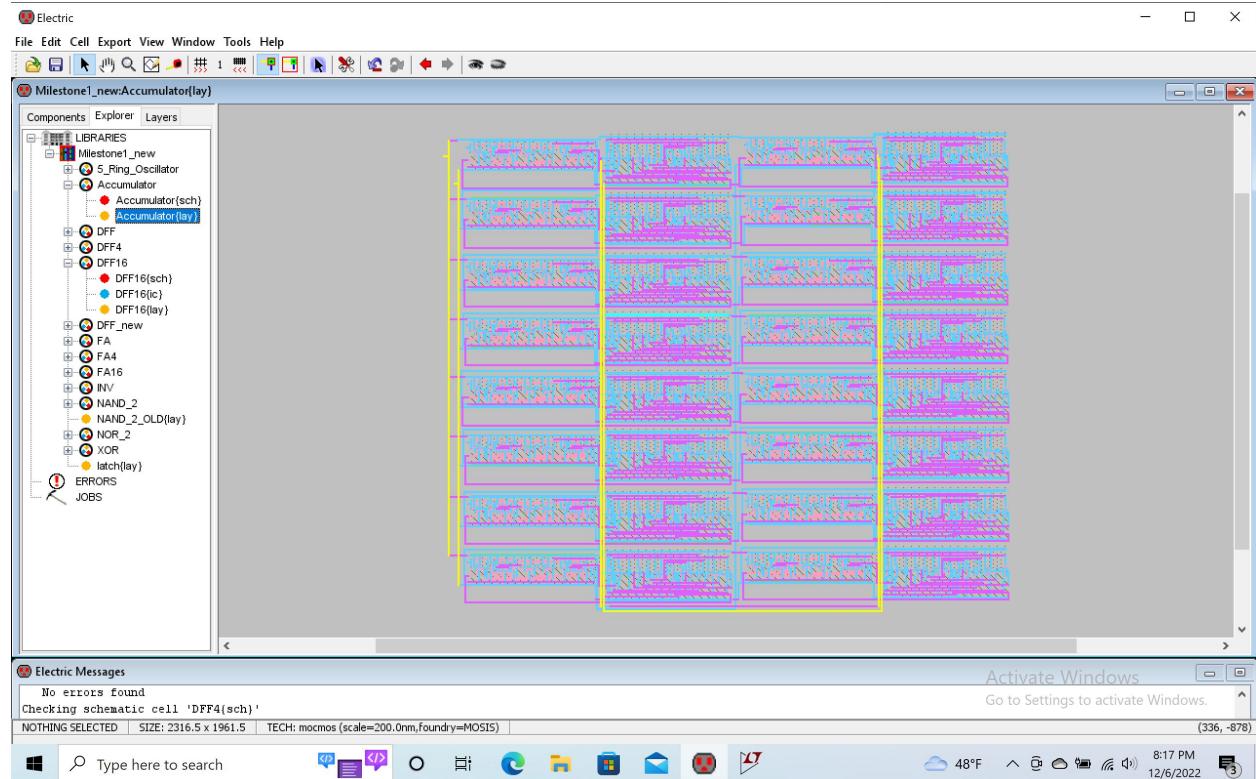


Accumulator Layout




Passing DRC+ERC+NCC

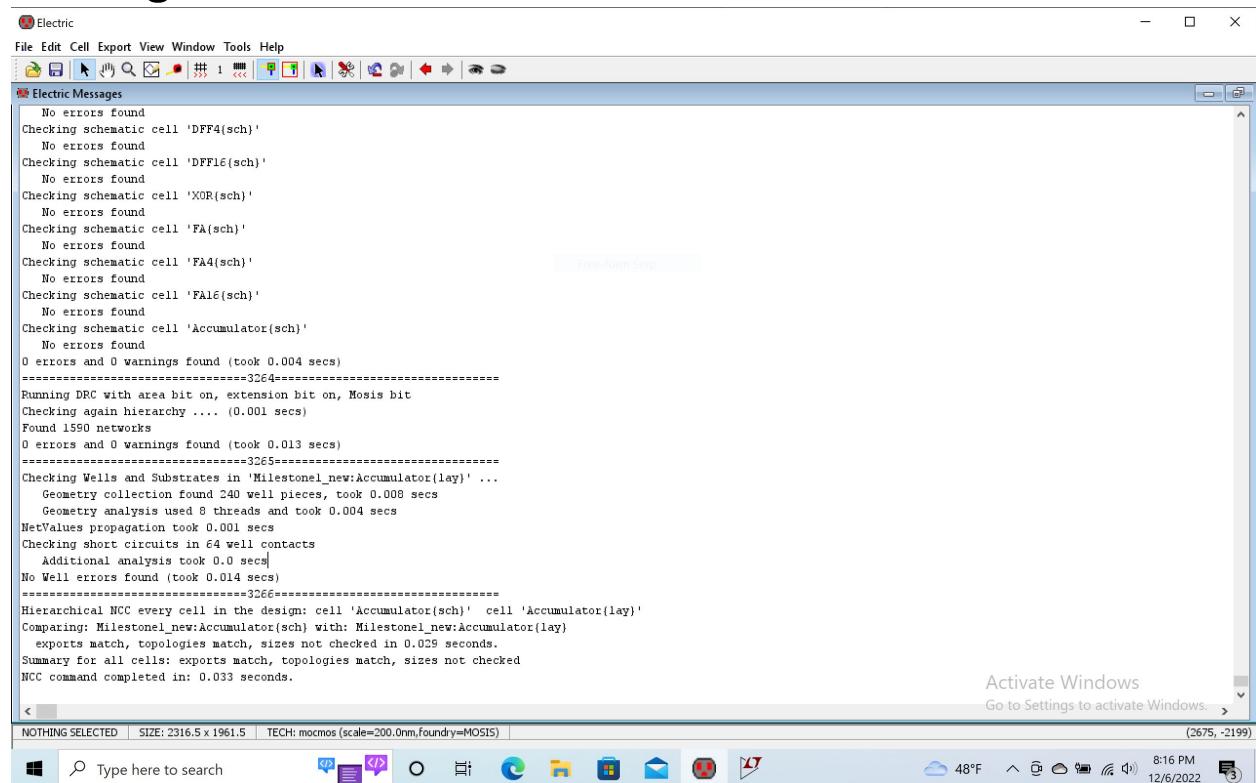

Inputs Simulation

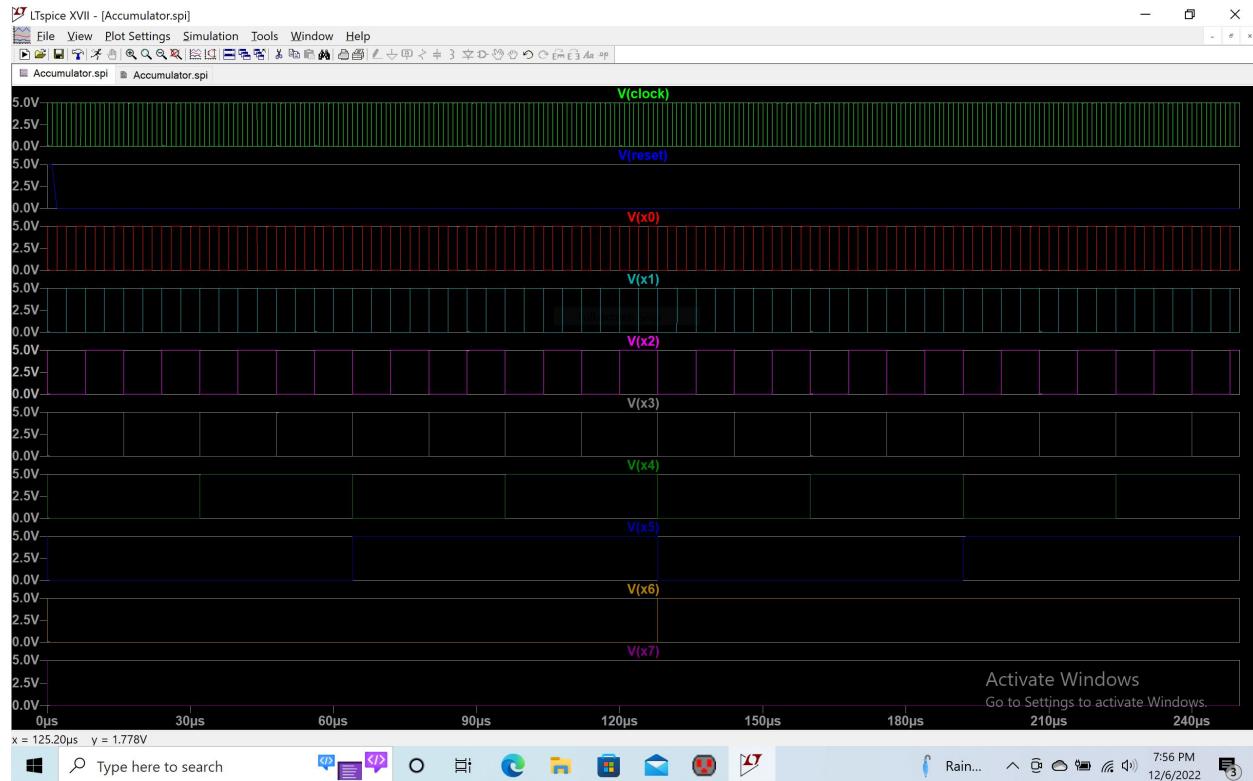

Outputs Simulation

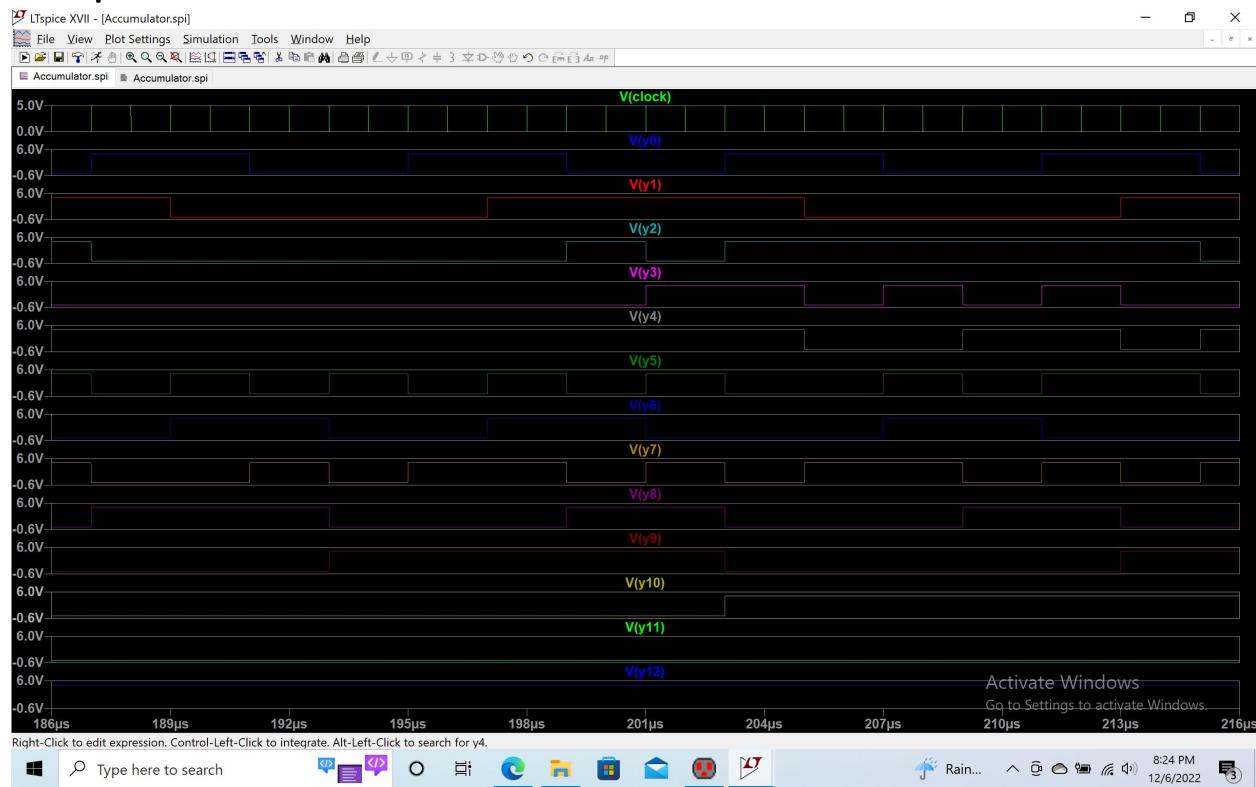

5050 Pass

